

LCLS BPMs

Patrick Krejcik

Steve Smith

Ron Johnson

Evgeny Medvedko

Till Straumann

Overview


- Requirements
- BPM Types
 - Striplines
 - Cavities
- BPM Processor Concept
- Status
- Planned Work

LCLS BPMs

- Measurement of transverse position of electron beam trajectory
- ~150 BPMs along the machine (injector, linac, LTU, undulator, dump)
- Positional resolution requirement 1..20 μ m @0.1nC (R~10mm)
- Two different physical devices
 - Striplines (5-10 μ m resolution)
 - Cavities (< 1 μ m resolution)
- Use existing linac striplines

Stripline BPM

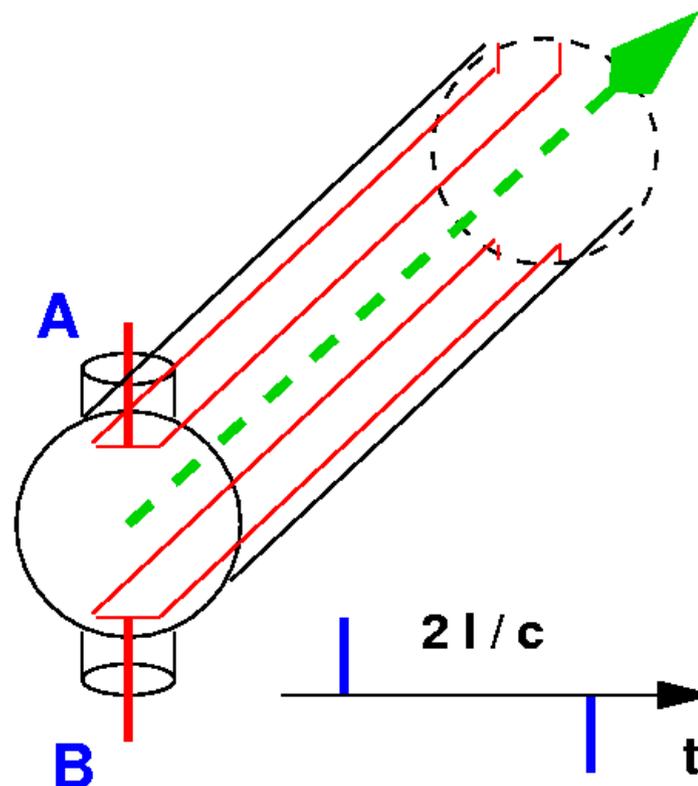- Short electron bunch induces wideband pulse doublet
- Positional information is small difference of large numbers ($\sim 5E-3$)
- $Y/R \sim 4 (A-B) Q$



Stripline BPM Electronics

■ Backend

- Wideband ADC (state of the art: 14bit, 100MSPS, 200MHz input signal BW)


■ Frontend

- Limit bandwidth (“ring a filter”)
- Set processing center frequency (undersample, mixer)
- Match signal level to ADC
- Optional: difference “A-B” in hybrid

■ Normalize to bunch charge (e.g., $(A-B)/(A+B)$)


■ Calibration (offset, gain)

Analog Frontend Electronics (Strip1)

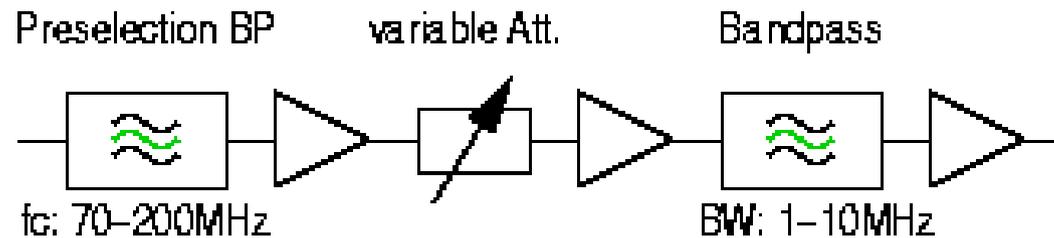

No conversion of processing freq.

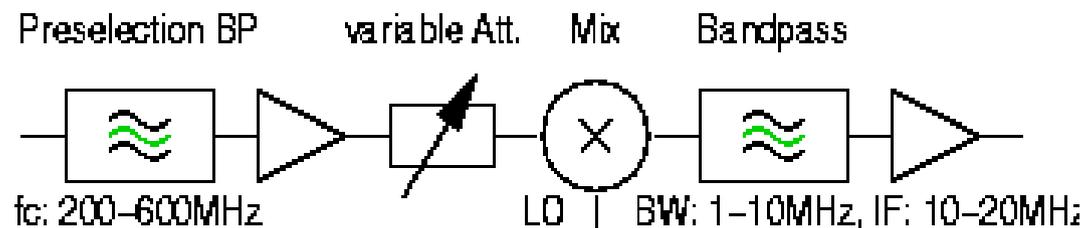- Simple; more sensitive to ADC and clock




Heterodyne receiver

- Higher freq. Possible; needs LO

Frontend Processor Options


■ Digital Difference

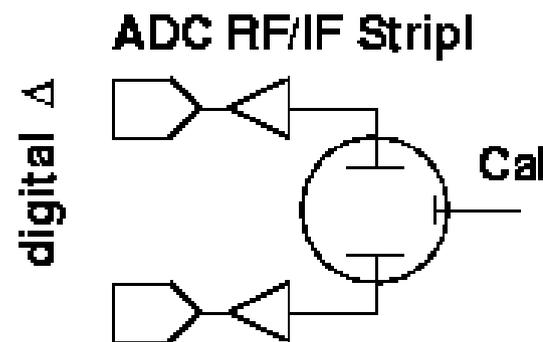- Easy gain/offset calibration
- Requires higher dynamic range
- More channels needed





■ Analog Difference

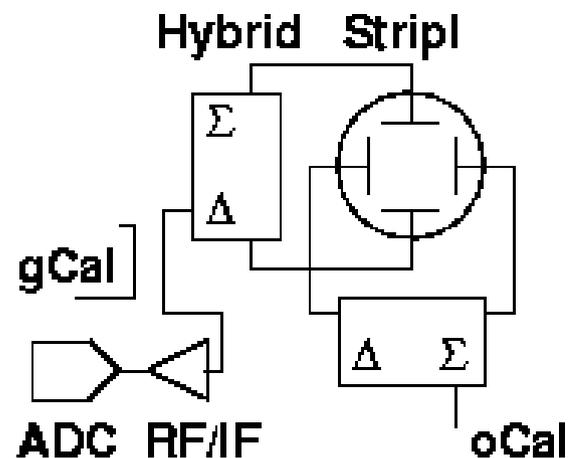- Less channels
- Bunch charge info needed
- Reduced dynamic range
- Relies on hybrid symmetry (?)



Calibration

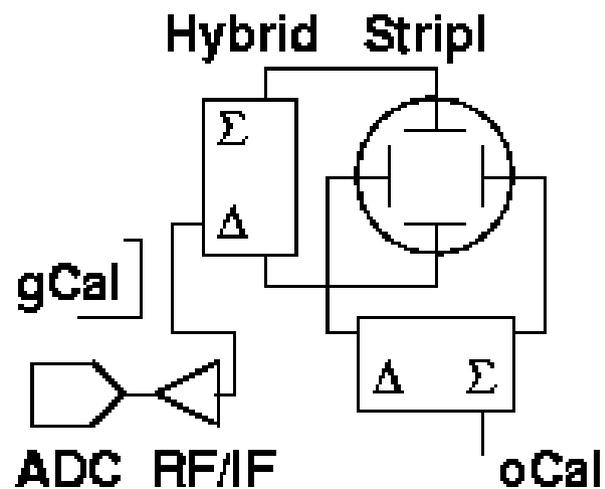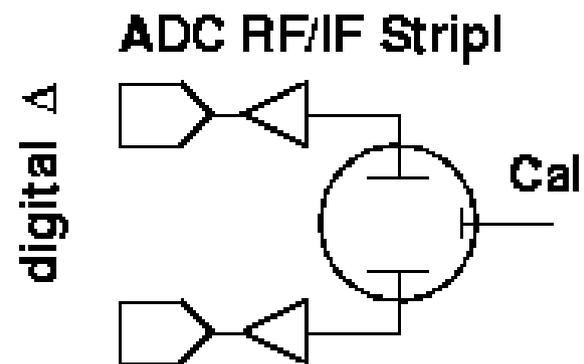- Inject calibration signal to orthogonal strips
 - Takes care of gain and offset
 - Sensitive to imbalance of active parts (diff. of big numbers)
- Inject to sum port of orthogonal hybrid
 - Relies only on symmetry of strips
 - Less sensitive (drift of active parts)
 - Separate gain cal. Needed




Important Design Parameters

- Processing frequency (cable losses, stripline response)
- Processing bandwidth (tradeoff analog SNR vs. processing gain to reduce digitizer noise)
- Linearity (if calculating difference in digital domain)
- Noise Figure (low bunch charge)


BPM Processor -- Controls

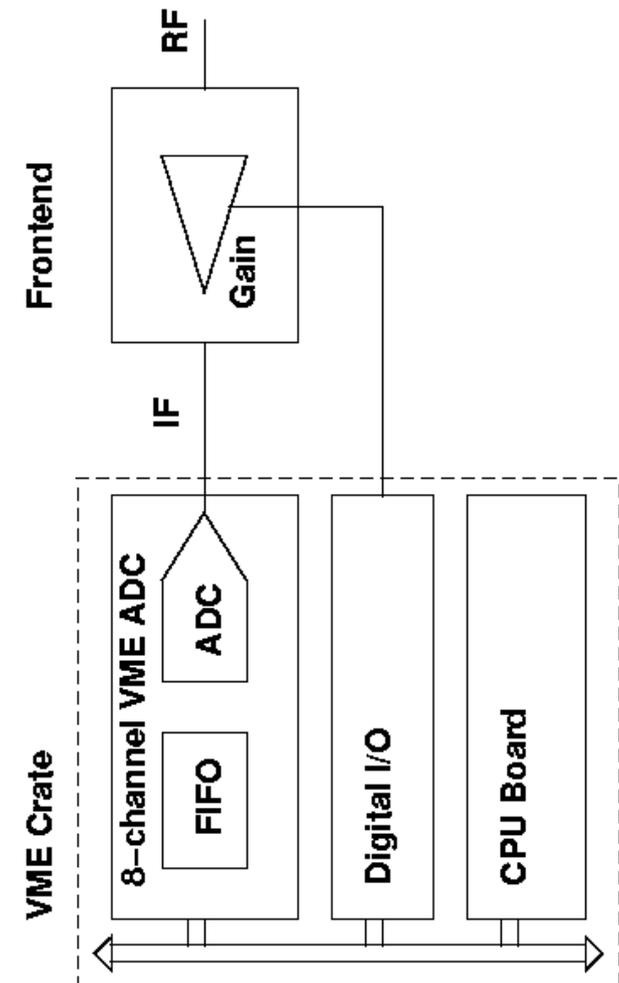- Commercial VME digitizer (8 channels/card)
- **Slow backplane**
- Digital I/O for gain control; calibration
- Ext. trigger
- “Scalar processor”
- Optional: digital receiver to reduce backplane & processing load



Cavity BPMs

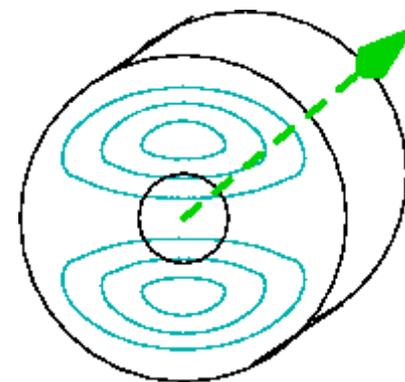- Excitation of dipole mode by off-center beam
- Sensitive to position and angle
- No response at center
- Reference cavity needed
 - Phase info (“up” vs. “down”)
 - Normalize to bunch charge
- Problem: suppression of monopole mode
- C- or X- band operation
- Complex Calibration (mechanical?)



Cavity BPM Processor

- Use same backend as for striplines (VME digitizer)
- “Vector processor” because phase info needed
- 2-stage heterodyne frontend
- Is a mechanical positioning subsystem necessary?
(work at ATF: 3 BPMs in a sophisticated mechanical positioning setup).

Status

- Understand critical design parameters and processing algorithms
- Conceptual design
- Identified VME digitizers. Evaluation modules ordered
- Prototype for a 140MHz (wrong freq.) analog front-end is being built (Smith)
- Looked at Libera solution. Doesn't seem to be useful for our application.

Next Months

- Evaluation of Echotek VME digitizer
- Prototype front-end for stripline BPMs
- Run tests on live beam
- Test “Hybrid solution”
- Test calibration schemes, stability